

- P13-36. Analyze the memory element in Fig. P13.36. Draw up a truth table assuming the input is a series of pulses and  $Q$  is initially 1. What function is performed by the AND gates?

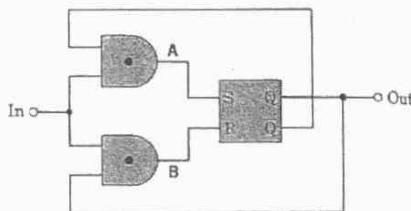


Figure P13.36 Memory element.

- P14-12. Use Boolean theorems to prove the following identities:

- $A + \bar{A}B = A + B$
- $ABC + ABC\bar{C} = AB$
- $(A + \bar{B})B = AB$
- $(A + B)(\bar{A} + C) = AC + \bar{A}B$

- P14-13. When writing equations for "programmed array logic" circuits, complicated expressions must be broken down into simple "sums-of-products" (like Eq. 14-6).

- (a) Write the following expression as a sum-of-products. Show the Boolean theorems used during each step of simplification.

$$[(A \cdot B \cdot \bar{C}) \cdot (\bar{A} \cdot B \cdot C) + \bar{A} \bar{B}] \cdot \bar{D}$$

- (b) Invert the result from part (a), and factor it into a sum-of-products, showing theorems used.

- P14-14. The function  $f = A + B$  is to be realized using only **NAND** gates. Use DeMorgan's theorems to express  $f$  in terms of  $\bar{C} \cdot \bar{D}$  where  $C$  and  $D$  can be expressed in terms of  $A$  and  $B$ . Draw the necessary logic circuit and check by constructing the truth table.

- P14-15. Analyze the logic circuit of Fig. P14.15 and determine  $f$  in terms of  $A$  and  $B$ . Simplify using Boolean algebra and check your result with a truth table.

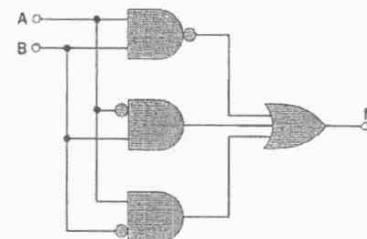


Figure P14.15

- P14-20. Given the logic function

$$f = \overline{AB} + \overline{A}\overline{B} + \overline{AB}$$

- Assuming the complements are available, simplify the function using DeMorgan's theorem and synthesize it using the basic gates.
- Assuming the complements are not available, simplify the function and synthesize it from five **NAND** gates.

Answer: (a)  $f = AB + BA$ .

- P14-24. Map the following functions and find the minimal sum-of-products form:

- $ABCD + A\bar{B}C + \bar{B}\bar{C}$
- $AB + \bar{A}\bar{B}CD + A\bar{B}C$

1. P13-36 R & S are alternatively turned on  $\Rightarrow$   
output switches on & off w/ each pulse.

Pulse #	Q <sub>n-1</sub>	A	B	Q <sub>n</sub>
1	1	0	1	0
2	0	1	0	1
3	1	0	1	0

2. P14-12 a.  $A + \bar{A}B = A(B + \bar{B}) + \bar{A}B = AB + A\bar{B} + \bar{A}B (+AB) = A(B + \bar{B}) + (A + \bar{A})B = (A + B)$  ✓  
 b.  $ABC + ABC\bar{C} = ABC(C + \bar{C}) = (AB)$  ✓  
 c.  $(A + \bar{B})B = AB + B\bar{B} = (AB)$  ✓  
 d.  $(A + B)(\bar{A} + C) = A\bar{A} + B\bar{A} + AC + BC = \bar{A}BC(C + \bar{C}) + AC(B + \bar{B}) + (A + \bar{A})BC = \bar{A}BC + \bar{A}B\bar{C} + ABC + A\bar{B}C = \bar{A}BC + \bar{A}B\bar{C} + ABC + A\bar{B}C = \bar{A}B(C + \bar{C}) + A(B + \bar{B})C$   $\bar{A}B + AC$  ✓


3. P14-13

a.  $[(ABC) \cdot (\bar{A}\bar{B}C) + \bar{A}\bar{B}] \cdot \bar{D}$   
 $[(A\bar{B}\bar{C}) \cdot (\bar{A} + B + \bar{C}) + \bar{A}\bar{B}] \cdot \bar{D}$  DeMorgan  
 $[\bar{A}\bar{B}\bar{C} + ABB\bar{C} + AB\bar{C}\bar{C} + \bar{A}\bar{B}] \cdot \bar{D}$  Distribution  
 $[\bar{A}\bar{B}\bar{C} + \bar{A}\bar{B}] \cdot \bar{D}$  Boole  
 $(ABC\bar{D} + \bar{A}\bar{B}\bar{D})$  Distribution

b.  $(ABC\bar{D} + \bar{A}\bar{B}\bar{D}) = \bar{A}\bar{B}\bar{C}\bar{D} + \bar{A}\bar{B}\bar{D}$  DeMorgan.  
 $(\bar{A} + \bar{B} + C + D) \cdot (A + B + D)$  DeMorgan  
 $\bar{A}B + \bar{A}\bar{B} + AC + BC + D$  Distribution

4. P14-14  $f = A + B = \overline{\overline{A} \cdot \overline{B}} = \overline{(\overline{A} \cdot \overline{A}) \cdot (\overline{B} \cdot \overline{B})}$

A	B	$\overline{A} \cdot \overline{B}$	$\overline{\overline{A} \cdot \overline{B}}$ $= A + B$
0	0	1	0
0	1	0	1
1	0	0	1
1	1	0	1

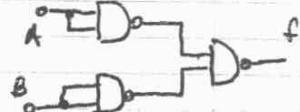



5. P14-15

$$f = \overline{AB} + \overline{AB} + AB \\ \therefore \overline{AB} + \overline{AB} + AB$$

A	B	$\overline{AB}$	$\overline{AB}$	$AB$	$f = \overline{AB}$
0	0	1	0	0	1
0	1	1	0	0	0
1	0	0	0	0	0
1	1	0	0	1	0

$$f = \overline{AB} + \overline{AB} + A\bar{B} \\ = \bar{A} + \bar{B} + \overline{AB} + A\bar{B} \\ = \bar{A}(1+B) + (1+A)\bar{B} \\ = \bar{A} + \bar{B} = \overline{AB}$$

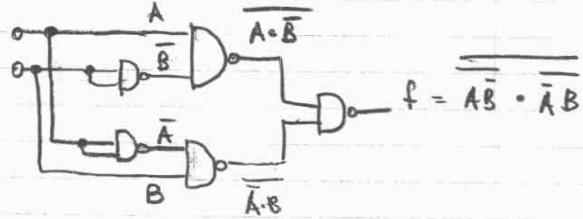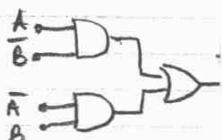6. P14-20  $f = \overline{AB} + \overline{A}\bar{B} + \bar{A}P$   
 $f = \overline{AB} - \overline{A}\bar{B} + \overline{AB}$   
 $= (\bar{A} + \bar{B})(A + B) + \overline{AB}$   
 $= \bar{A}\bar{A} + \bar{A}B + A\bar{B} + BB + \overline{AB}$   
 $= \bar{A}\bar{B} + AB$   
 $= \overline{AB} - \overline{AB}$  (w/ NANDS)



7. P14-24

CD	AB	00 01 11 10
00	1	1
01	1	1
11	1	1
10	0	1

a)  $f = ABC\bar{D} + A\bar{B}C + \bar{B}\bar{C}$   
 $= A\bar{B} + \bar{B}\bar{C} + A\bar{C}\bar{D}$

CD	AB	00 01 11 10
00	1	1
01	1	1
11	1	1
10	0	1

b)  $f = AB + \bar{A}\bar{B}CD + A\bar{B}C$   
 $= AB + AC + \bar{B}CD$