

1.19, 1.22, 2.11, 2.22,
2.33, 2.34, 3.8, 3.21

Engineering II
Electrical Circuit Analysis
Assignment 1 Solutions


LAM
9.5.05

①

1.19 v, i @ terminals of device given

(a) Sketch $p(t)$ for $0 \leq t \leq 10$ s

t (s)	v (V)	i (A)	p (W)
$0 \leq t \leq 1$	5	$20t$	$100t$
$1 \leq t \leq 2$	0	20	0
$2 \leq t \leq 3$	0	20	0
$3 \leq t \leq 4$	-5	$80-20t$	$-400+100t$
$4 \leq t \leq 5$	-5	$80-20t$	$-400+100t$
$5 \leq t \leq 6$	5	$-120+20t$	$-600+100t$
$6 \leq t \leq 7$	5	$-120+20t$	$-600+100t$
$7 \leq t \leq 10$	0	20	0

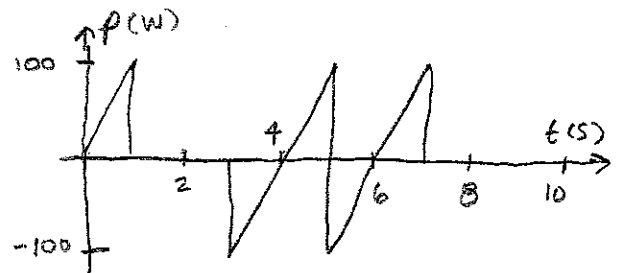

(b) Calculate area under curve from $0 \rightarrow t$ for $t = 1, 6, 10$ s.

$$w(1) = \frac{1}{2}(1)(100) = 50 \text{ J}$$

$$w(6) = 2 \cdot \left(\frac{1}{2}\right)(1)(100) - 2 \cdot \left(\frac{1}{2}\right)(1)(100) = 0$$

$$w(10) = 3 \cdot \left(\frac{1}{2}\right)(1)(100) - 2 \cdot \left(\frac{1}{2}\right)(1)(100) = 50 \text{ J}$$

② 1.22 v, i of charging battery given

(a) Calculate total q transferred to battery (area under curve $q = \int i dt$) (use boxes given)

$$q = \frac{1}{2}(5000)(6) + 5000(6) + \frac{1}{2}(10000)(6) + 15000(8) + \frac{1}{2}(5000)(8) = \boxed{215,000 \text{ C}}$$

(b) Calculate total energy transferred to the battery $w = \int p dt = \int v i dt$

$$v = \begin{cases} 0.2(10^{-3})t + 8 & 0 \leq t \leq 20 \text{ ks} \\ 12 & t \geq 20 \text{ ks} \end{cases}$$

$$i = \begin{cases} 20 - 1.2(10^{-3})t & 0 \leq t \leq 5 \text{ ks} \\ 17 - 0.16(10^{-3})t & 5 \text{ ks} \leq t \leq 15 \text{ ks} \\ 3.2 - 1.6(10^{-3})t & 15 \text{ ks} \leq t \leq 20 \text{ ks} \\ 0 & t \geq 20 \text{ ks} \end{cases}$$

$$\boxed{15 \text{ ks} \leq t \leq 20 \text{ ks}} \quad p = 256 - 6.4(10^{-3})t - 3.2(10^{-7})t^2$$

$$w = \int_{15 \text{ ks}}^{20 \text{ ks}} p dt = \left[256t - \frac{6.4(10^{-3})t^2}{2} - \frac{3.2(10^{-7})t^3}{3} \right]_{15 \text{ ks}}^{20 \text{ ks}} = \boxed{226.7 \text{ kJ}}$$

$$\boxed{0 \leq t \leq 5 \text{ ks}} \quad p = 160 - 5.6(10^{-3})t - 2.4(10^{-7})t^2$$


$$w = \int_0^{5 \text{ ks}} p dt = \left[160t - \frac{5.6(10^{-3})t^2}{2} - \frac{2.4(10^{-7})t^3}{3} \right]_0^{5 \text{ ks}} = \boxed{720 \text{ kJ}}$$

$$\boxed{5 \text{ ks} \leq t \leq 15 \text{ ks}} \quad p = 136 - 1.4(10^{-3})t - 1.2(10^{-7})t^2$$

$$w = \int_{5 \text{ ks}}^{15 \text{ ks}} p dt = \left[136t - \frac{1.4(10^{-3})t^2}{2} - \frac{1.2(10^{-7})t^3}{3} \right]_{5 \text{ ks}}^{15 \text{ ks}} = \boxed{1090 \text{ kJ}}$$

$$w_{\text{total}} = 720 + 1090 + 226.7 = \boxed{2036.7 \text{ kJ}}$$

③ 2.11 Find power developed (supplied)

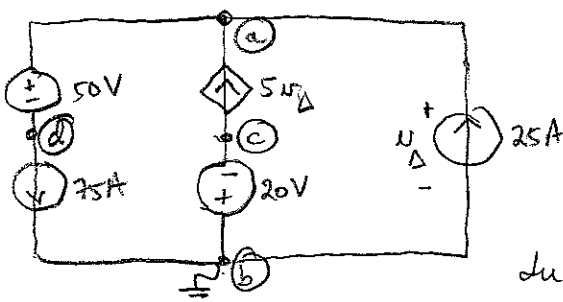

$$\sum i = 0 = -75 + 5V_A + 25 \Rightarrow V_A = 10 \text{ V}$$

$$V_A = V_a - V_b = 10 \text{ V} \quad \text{Let } V_b = 0 \text{ (ground)}$$

In the middle branch, $V_c = -20 \text{ V}$, so the voltage drop across the $5V_A$ current source, $V_a - V_c = 30 \text{ V}$

In left branch, $V_d = V_a - 50 = -40 \text{ V}$.

Elements delivering power have $\begin{matrix} + \\ \bigcirc \\ - \end{matrix} \leftarrow i$, which are:

75 A current source w/ $p = (40)(75) = 3000 \text{ W}$,


$5V_A = 50 \text{ A}$ current source w/ $p = (30)(50) = 1500 \text{ W}$,

& 25 A current source w/ $p = (10)(25) = 250 \text{ W}$


$$\therefore \text{Power supplied} = 3000 + 1500 + 250 = \boxed{4750 \text{ W}}$$

4. 2.22


a) Plot i vs V

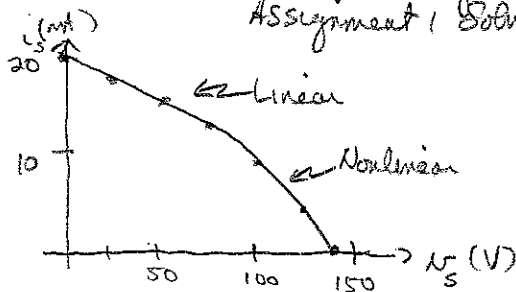

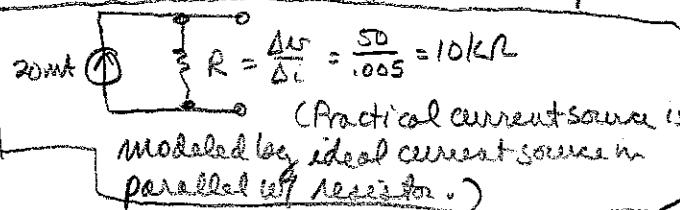b) Construct a model for the linear portion



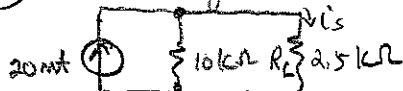c) Find i_s for $R_L = 2.5\text{k}\Omega$



By current $\div$,
 $i_{2.5\text{k}} = \frac{10}{10+2.5} (20\text{mA}) = 16\text{mA}$





$V_{oc} = (20\text{mA})(10\text{k}) = 200\text{V}$


e) Actual $V_{oc} = 140\text{V}$ (when $i_s = 0$)

f) Device is nonlinear & has varying values for R depending on i_s / V_s .

5. 2.33

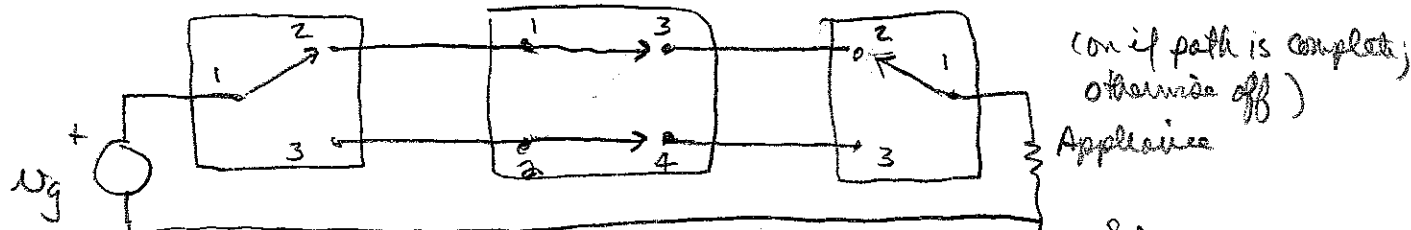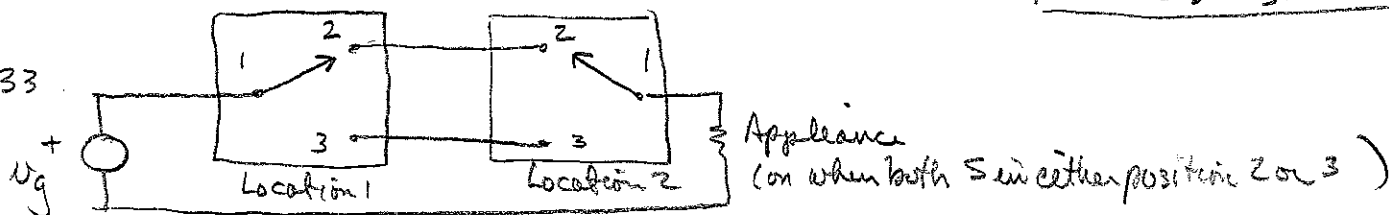


6. 2.34

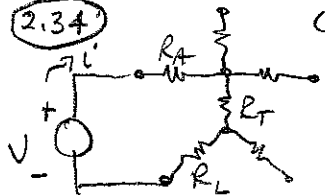

(Fig 2.25)
 $V = 250\text{V}$
 $R_A = 400\Omega$
 $R_T = 50\Omega$
 $R_L = 200\Omega$

so $\sum V = 0 = 250 - iR_A - iR_T - iR_L$
 $250 = i(400 + 50 + 200) = i(650)$
so $i = 385\text{mA}$ dangerous.

7. 3.18

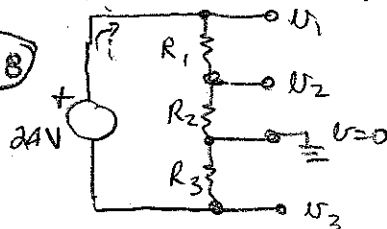

Set $V_1 = 12\text{V}$
 $V_2 = 6\text{V}$
 $V_3 = -12\text{V}$

$P = 36\text{W} \Rightarrow V i = 36 = 24i$ or $i = \frac{3}{2}\text{A}$

Then $R_1 = \frac{\Delta V}{i} = \frac{6}{3/2} = 4\Omega$ (ΔV = drop across given resistor)


$R_2 = \frac{\Delta V}{i} = \frac{6}{3/2} = 4\Omega$

$R_3 = \frac{\Delta V}{i} = \frac{12}{3/2} = 8\Omega$

2.38

$R_{space} = 1\text{M}\Omega$, $i = 3\text{mA} \Rightarrow$
 $V = R_{space} i = 3\text{kV}$

8. 3.21

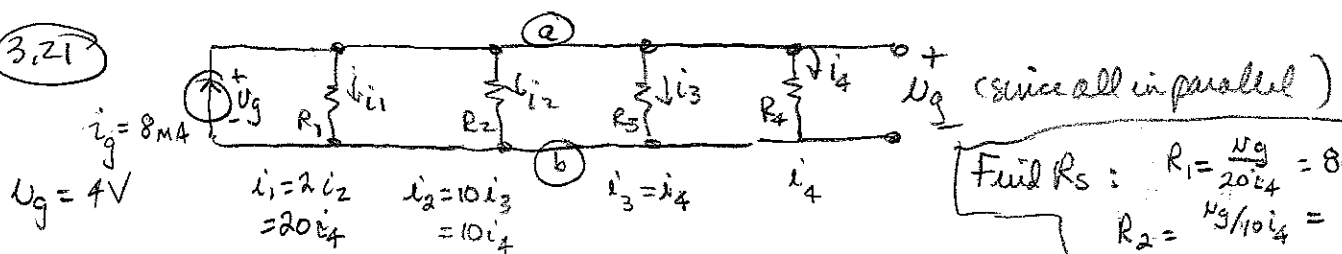

Find R_s : $R_1 = \frac{V_g}{20i_4} = 800\Omega$

$R_2 = \frac{V_g}{10i_4} = 1.6\text{k}\Omega$

$R_3 = R_4 = \frac{V_g}{i_4} = 16\text{k}\Omega$

$\sum i = 0 = 8\text{mA} - 20i_4 - 10i_4 - i_4 - i_4 \Rightarrow 32i_4 = 8\text{mA}$ or $i_4 = 0.25\text{mA}$