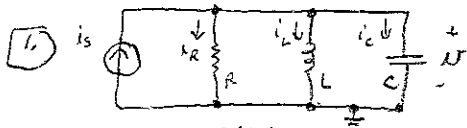


Engineering II Assignment Solutions



$i_s(t) = I_0 \delta(t)$

$$\sum i = 0 \Rightarrow \frac{V}{R} + \frac{1}{L} \int V dt + C \frac{dV}{dt} = I_0 \delta(t) \quad \text{let } V = \frac{d\lambda}{dt}$$

$$\frac{d^2 \lambda}{dt^2} + \frac{1}{RC} \frac{d\lambda}{dt} + \frac{1}{LC} \lambda = \frac{I_0}{C} \delta(t)$$

Homogeneous: set source = 0 ; $\lambda_{test} = A e^{st} \Rightarrow s^2 + \frac{1}{RC}s + \frac{1}{LC} = 0$

$R=L=C=1 \Rightarrow s = -\frac{1}{2} \pm j\frac{\sqrt{3}}{2}$ so $\lambda_h = A e^{-t/2} \cos(\frac{\sqrt{3}}{2}t + \phi)$; $\lambda_p = 0$ (always true for impulses)

$IC: \int_0^+ \frac{d^2 \lambda}{dt^2} dt + \frac{1}{RC} \int_0^+ \frac{d\lambda}{dt} dt + \frac{1}{LC} \int_0^+ \lambda dt = \frac{I_0}{C} \int_0^+ \delta(t) dt \Rightarrow \frac{d\lambda}{dt} \Big|_0^+ - \frac{d\lambda}{dt} \Big|_0^- + \frac{1}{RC} \lambda \Big|_0^+ - \frac{1}{RC} \lambda \Big|_0^- + 0 = \frac{I_0}{C} \Rightarrow \frac{d\lambda}{dt} \Big|_0^+ + \frac{1}{RC} \lambda(0^+) = \frac{I_0}{C}$

$\left[\int_0^+ \lambda dt = 0 \text{ as long as } \lambda(0^+) \text{ is finite} \right]$ For finite $\frac{d\lambda}{dt}$, $\lambda(0^+) = 0 \Rightarrow \frac{d\lambda}{dt} \Big|_{t=0^+} = \frac{I_0}{C}$

$\lambda(0^+) = 0 = A \cos \phi \Rightarrow \cos \phi = \pm \pi/2$ (choose $-\pi/2$)

$\frac{d\lambda}{dt} \Big|_{t=0^+} = \frac{I_0}{C} = -\frac{1}{2} A \sin \phi - \frac{\sqrt{3}}{2} A \cos \phi \Rightarrow A = \frac{2}{\sqrt{3}} \frac{I_0}{C} \Rightarrow \lambda(t) = \frac{2}{\sqrt{3}} I_0 e^{-t/2} \cos(\frac{\sqrt{3}}{2}t - \pi/2) u(t)$

$v(t) = \frac{d\lambda}{dt} = -\frac{1}{\sqrt{3}} I_0 e^{-t/2} \cos(\frac{\sqrt{3}}{2}t - \pi/2) u(t) - \frac{1}{3} I_0 e^{-t/2} \sin(\frac{\sqrt{3}}{2}t - \pi/2) u(t) + \frac{2}{\sqrt{3}} I_0 e^{-t/2} \cos(\frac{\sqrt{3}}{2}t - \pi/2) \delta(t)$

2. 14.6 a. $f_c = \frac{\omega_c}{2\pi} = 7.958 \text{ kHz}$ b. $\frac{1}{RC} = 50(10^3) \Rightarrow R = 40 \Omega$

c. $Z(s) = \frac{R_{eq}}{s + R_{eq}C}$, $R_{eq} = \frac{R R_L}{R + R_L} \Rightarrow s = -\frac{1}{R_{eq}C} = -\omega_c \Rightarrow R_L = 860 \Omega$


d. For $\omega \rightarrow 0$, $Z_c = \frac{1}{j\omega C} \rightarrow \infty \Rightarrow V_i = \frac{V_o}{R_L} = \frac{R_L}{R + R_L} = 0.9524$

3. 14.17 a. $\omega_0 = \sqrt{\frac{1}{LC}} = 25 \text{ krad/s} \Rightarrow f_0 = \frac{\omega_0}{2\pi} = 3.979 \text{ kHz}$



$\frac{V_o}{V_i} = \frac{R_L}{R + R_L + j(\omega L - \frac{1}{\omega C})} = \frac{R_L / (R + R_L)}{1 + jQ(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega})}$

b. $Q = \frac{\omega_0 L}{R + R_L} = 5$

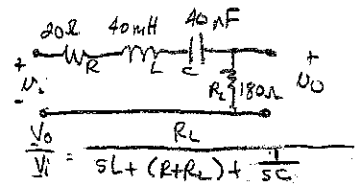c. $\omega_{c1} = \omega_0 [-\frac{1}{2Q} + \sqrt{1 + (\frac{1}{2Q})^2}] = 22.6 \text{ krad/s}$ d. $\omega_{c2} = \omega_0 [\frac{1}{2Q} + \sqrt{1 + (\frac{1}{2Q})^2}] = 27.6 \text{ krad/s}$





4. Plot amplitude & phase of 14.6

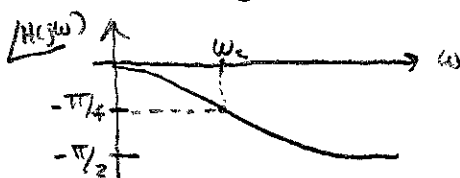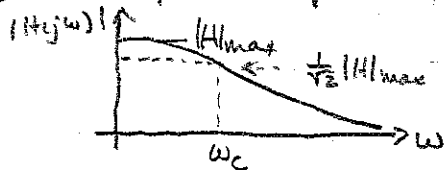

$$H(j\omega) = \frac{R_L \| Z_c}{R + R_L \| Z_c} = \frac{R_L / j\omega C}{R + \frac{R_L / j\omega C}{1 + j\omega(R_L / j\omega C)}} = \frac{R_L}{R + R_L} \frac{1}{1 + j\omega \left(\frac{R R_L C}{R + R_L} \right)}$$

$$\angle H_{max} = \frac{R_L}{R + R_L}$$

5. Plot amplitude & phase of 14.17

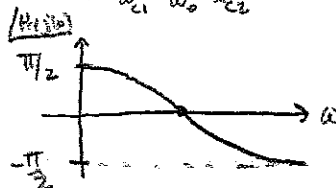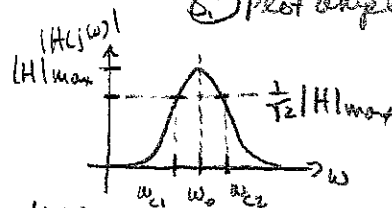

$$H(j\omega) = \frac{R_L}{R + R_L} \frac{j\omega}{1 + jQ(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega})}$$

$$= K \frac{j\omega}{\sqrt{1 + [Q(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega})]^2}} \left[\frac{\pi}{2} - \tan^{-1} \left[Q \left(\frac{\omega}{\omega_0} - \frac{\omega_0}{\omega} \right) \right] \right]$$

$$|H|_{max} = K = \frac{R_L}{R + R_L}$$