

P3-25. Explaining your reasoning and stating any simplifying assumptions, predict current I in Fig. P3.25.

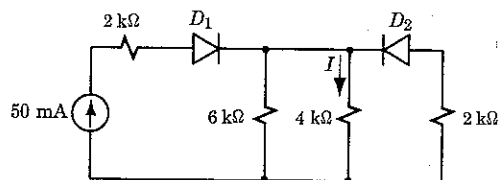


Figure P3.25

P3-41. In Fig. P3.41, when voltage $v_1 = V_m(0.5 + \sin \omega t)$ V, the high-resistance dc voltmeter VM reads 70 V.

- What functions are performed by each section of the circuits?
- How is v_2 related to v_1 ? Show v_1 , v_2 , and v_3 on the same graph.
- Determine V_m and define the function of this instrument.

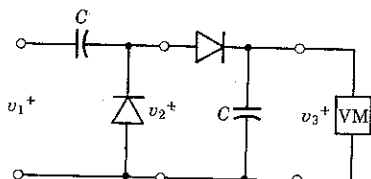


Figure P3.41

P13-36. Analyze the memory element in Fig. P13.36. Draw up a truth table assuming the input is a series of pulses and Q is initially 1. What function is performed by the AND gates?

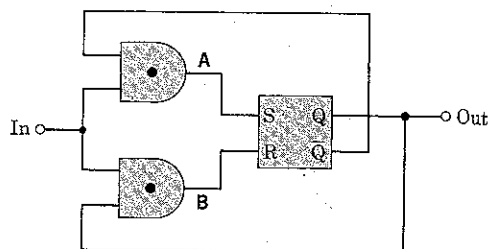


Figure P13.36 Memory element

P14-12. Use Boolean theorems to prove the following identities:

- $A + \bar{A}B = A + B$
- $ABC + \bar{A}BC = AB$
- $(A + \bar{B})B = AB$
- $(A + B)(\bar{A} + C) = AC + \bar{A}B$
- $(A + C)(A + D)(B + C)(B + D) = AB + CD$

P14-13. When writing equations for "programmed array logic" circuits, complicated expressions must be broken down into simple "sums-of-products" (like Eq. 14-6).

- Write the following expression as a sum-of-products. Show the Boolean theorems used during each step of simplification.

$$[(A \cdot B \cdot \bar{C}) \cdot (\bar{A} \cdot B \cdot C) + \bar{A}B] \cdot \bar{D}$$

- Invert the result from part (a), and factor it into a sum-of-products, showing theorems used.

P14-14. The function $f = A + B$ is to be realized using only **NAND** gates. Use DeMorgan's theorems to express f in terms of $\bar{C} \cdot \bar{D}$ where C and D can be expressed in terms of A and B . Draw the necessary logic circuit and check by constructing the truth table.

P14-15. Analyze the logic circuit of Fig. P14.15 and determine f in terms of A and B . Simplify using Boolean algebra and check your result with a truth table.

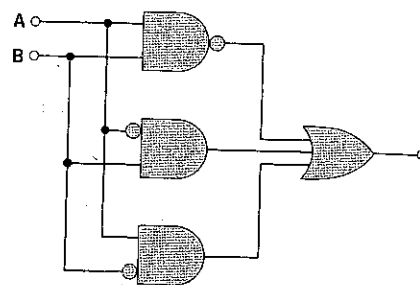


Figure P14.15

P14-20. Given the logic function

$$f = \overline{AB} + \overline{\bar{A}B} + \bar{A}B$$

- Assuming the complements are available, simplify the function using DeMorgan's theorem and synthesize it using the basic gates.
- Assuming the complements are not available, simplify the function and synthesize it from five **NAND** gates.

Answer: (a) $f = AB + \bar{A}B$.

P14-24. Map the following functions and find the minimal sum-of-products form:

- $ABCD + \bar{A}BC + \bar{B}\bar{C}$
- $AB + \bar{A}BCD + \bar{A}BC$
- $\bar{A}(C + D) + \bar{A}BC + \bar{A}\bar{B}\bar{C}\bar{D}$
- $\bar{A}BCD + \bar{A}BCD + \bar{B}CD + \bar{B}C$