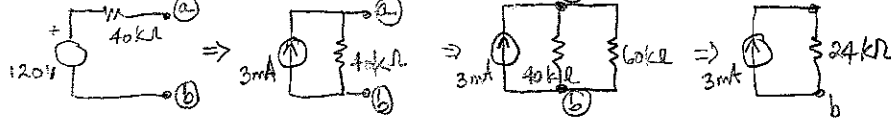


4.56a, 4.61, 4.69,
4.75, 4.85, 4.90, 4.94



Engineering 11 Electrical Circuit Analysis Assignment 3 Solutions

2005
LAM

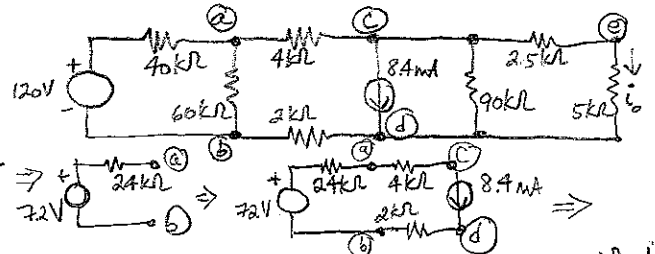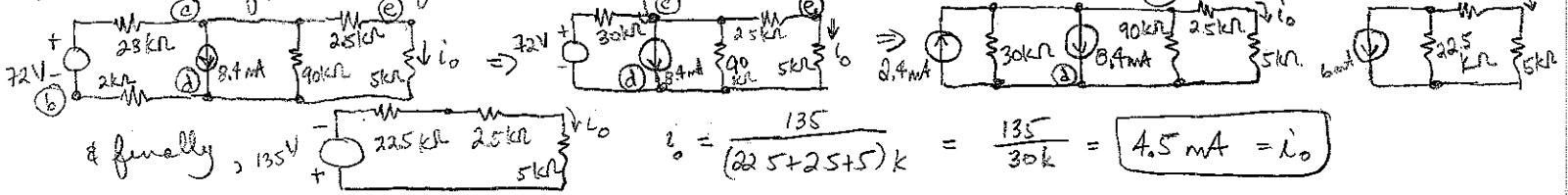1. 4.56a Use source transformation to find i_o .



Reattach RHS of circuit after combining $24k\Omega + 4k\Omega$



2. 4.61 Find the Thevenin equivalent @ terminals a,b.


Use $Y \rightarrow \Delta$ transformation.

$$R_{12} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_3} = \frac{200}{12} = \frac{50}{3} \Omega$$

$$R_{23} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_1} = \frac{200}{8} = \frac{50}{2} \Omega$$

$$R_{31} = \frac{R_1 R_2 + R_2 R_3 + R_3 R_1}{R_2} = \frac{200}{5.2} = \frac{500}{13} \Omega$$

Then for $V_T = V_{oc}$:

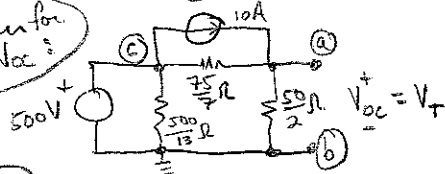


$$V_C = 500V$$


$$V_b = 0V$$

$$V_a = V_{oc} = \text{unknown}$$
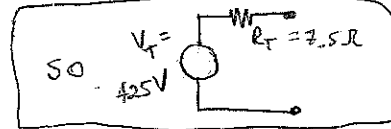
$$\sum i = 0 = 10 + \frac{500 - V_a}{(75/7)} - \frac{V_a}{(50/2)} = 0 \Rightarrow V_a = V_{oc} = 425V = V_T$$



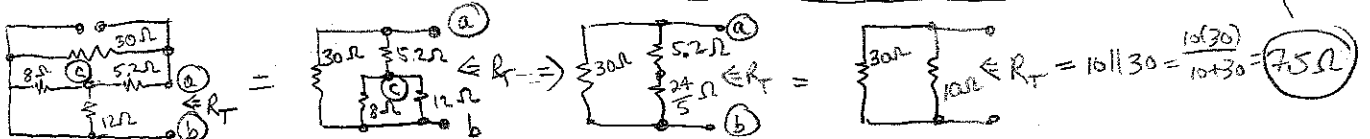For R_T
Deactivate sources
look into a,b &
find equiv. R



3. 4.69 VM reads 5.5 V. What is resistance of VM? ⑤ % error in voltage measurement?

(VM places R_m in parallel w/ 1.3kΩ resistor.)

Actual voltage: (note i_b = loop current I_b)

$$\sum i = 0 = 12 - 30k I_1 - 70k(I_1 - I_b) = 0$$

$$\text{loop 1 } \sum i = 0 = -1k I_b - 0.7 - 1.3k(I_b + 43I_b) - 70k(I_b - I_1)$$

$$\Rightarrow 100k I_1 - 70k I_b = 12$$

$$70k I_1 - [71k + 44(1.3k)] I_b = 0.7$$

$$\Rightarrow \text{using MATLAB} \Rightarrow \begin{bmatrix} I_1 \\ I_b \end{bmatrix} = \begin{bmatrix} \dots \\ \dots \end{bmatrix} \Rightarrow \text{Error} = \frac{5.5611 - 5.5}{5.5611} \approx 1.1\%$$

To find R_m , replace 1.3k resistor by $R_{eq} = 1.3k \parallel R_m$.

$$\text{so } 100k I_1 - 70k I_b = 12$$

$$70k I_1 - [71k + 44(R_{eq})] I_b = 0.7$$


and we also need $V_o = 5.5 = 44 R_{eq} I_b$; sub into for R_{eq} .

$$\Rightarrow \text{using MATLAB} \Rightarrow \begin{bmatrix} I_1 \\ I_b \end{bmatrix} = \begin{bmatrix} \dots \\ \dots \end{bmatrix}$$

$$\text{so } R_{eq} = \frac{5.5}{44 I_b} = 1.25k\Omega$$

$$\text{Then use } R_{eq} = \frac{1.3k R_m}{1.3k + R_m}$$


$$\Rightarrow R_m = 32.5k\Omega$$

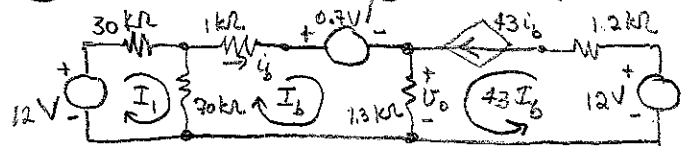

4. 4.75 Adjust R_o until $P_{R_o} = 250 \text{ W}$.

$$P_{R_o} = \frac{V_o^2}{R_o} = I_o^2 R_o$$

Start w/ source transformations:

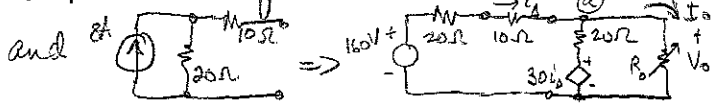


$$\text{So } \frac{160 - V_o}{30} - \frac{V_o - (160 - V_o)}{20} - \frac{V_o}{R_o} = 0$$

solving quadratic, $V_o = 75, 25$

$$\sum i = 0 = \frac{160 - V_o}{20} - \frac{V_o - 30i_\Delta}{20} - \frac{V_o}{R_o} = 0 ; i_\Delta = \frac{160 - V_o}{30}$$


$$R_o = \frac{V_o^2}{P_{R_o}} = \frac{V_o^2}{250}$$
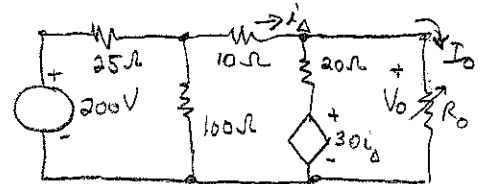
$$R_o = V_o^2 / 250 = 22.5 \Omega, 2.5 \Omega$$



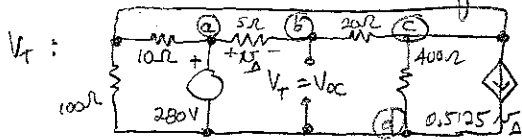5. 4.85 Adjust R_o for maximum power transfer.

Find R_o . Find Thevenin equivalent of all except R_o .




when R_o is removed, $i_\phi \rightarrow 0$
 $\Rightarrow$ voltage source across the top of the circuit $\rightarrow$ S.C.

$V_a = 280 \text{ V}$; collapse nodes abc into supernode.

$$\sum i = 0 = -\frac{V_c}{100} - \frac{V_c - 280}{10} - \frac{V_c}{400} - \frac{V_c - 280}{25} - 0.5125V_\Delta = 0 ; V_\Delta = \frac{5}{25}(280 - V_c) \Rightarrow V_c = 210 \text{ V}, V_\Delta = 14 \text{ V}$$
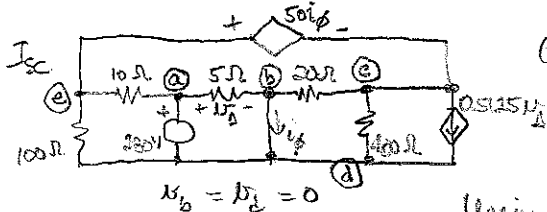
$$\text{so } V_T = V_{oc} = 280 - V_\Delta = 266 \text{ V}$$



Consider cc as a supernode.


$$\frac{V_b}{100} + \frac{V_c - 280}{10} + 0.5125V_\Delta + \frac{V_c}{400} + \frac{V_c}{20} = 0 ; \text{Note } V_\Delta = 280$$

$$\text{Supernode eq: } V_c + 50i_\phi = V_c ; \text{ and } i_\phi = \frac{280 - 0 + V_c - 0}{5 + \frac{20}{20}}$$

$$\text{Using MATLAB, } V_c = -968 \text{ V and } V_c = -588 \text{ V} \Rightarrow i_\phi = I_{sc} = 7.6 \text{ A}$$


Thevenin equiv:
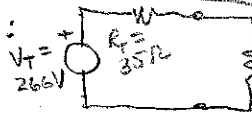
$$R_T = \frac{V_{oc}}{I_{sc}} = 35 \Omega$$



$R_o = 35 \Omega$ for max power transfer ($R_o = R_T$)



6. 4.90

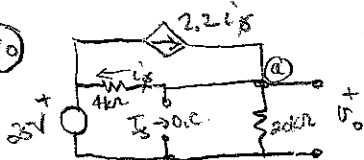

$$\sum i = 0 = 2.2i_\phi - i_\phi - \frac{V_o}{20k} ; i_\phi = \frac{V_o - 25}{4k}$$

$$\Rightarrow R_o | V_S = 30 \text{ V}$$

$$V_o |_{\text{total}} = 30 + 20 = 50 \text{ V}$$

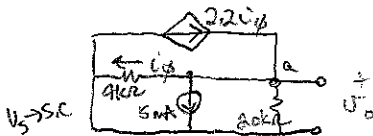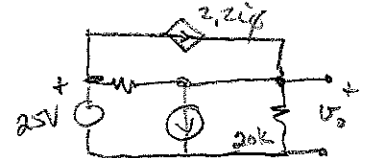


$$\sum i = 0 = 2.2i_\phi - i_\phi - 5 \text{ mA} - \frac{V_o}{20k} = 0$$

$$i_\phi = \frac{V_o}{4k} \Rightarrow R_o | I_S = 20 \text{ V}$$

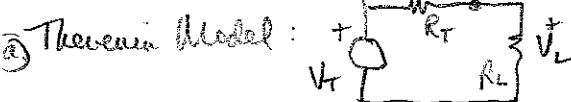7. 4.94 $V_{\text{no load}} = 75 \text{ V}$; $V_{20k} = 60 \text{ V}$

no load $\Rightarrow R_T \rightarrow \infty$ (O.C.) $\Rightarrow V_L = V_T = 75 \text{ V}$

$$V_L = 60 = \frac{R_L}{R_T + R_L} V_T = \frac{20}{R_T + 20} (60) \Rightarrow R_T = 5 \Omega$$



$$V_o = \frac{R_L}{R_T + R_L} V_T \Rightarrow V_T = (1 + \frac{R_T}{R_L}) V_o \Leftrightarrow \frac{R_T}{R_L} = \frac{V_T}{V_o} - 1 \Rightarrow R_T = (\frac{V_T}{V_o} - 1) R_L$$