
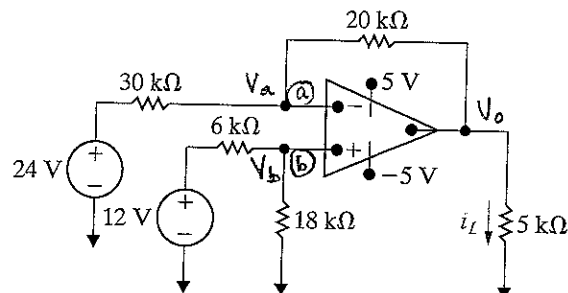


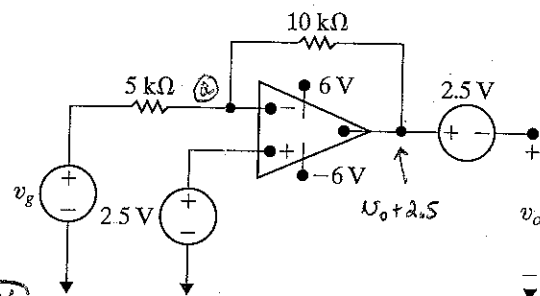1. 5.8 Find i_L in μA .
 $V_b = V_a$
 $\Rightarrow V_a = 9V; V_o = -1V$
 $\sum i_a = 0 = \frac{24 - V_a}{30k} - \frac{V_a - V_o}{20k}$
 $\sum i_b = 0 = \frac{12 - V_b}{6k} - \frac{V_b}{18k}$
 $\Rightarrow i_L = \frac{V_o}{5k} = -200 \mu A$




2. 5.9 $-5 < v_o < 5$ for $0 < v_g < 5V$. Note $V_a = 2.5V$.
 (a) Sketch v_o vs v_g .
 $\sum i_a = 0 = \frac{v_g - 2.5}{5k} - \frac{2.5 - (v_o + 2.5)}{10k}$
 (b) Yes ✓




3. 5.23 (a) For $v_g = 4V$, find v_o . By V_i , $v_b = v_a = \frac{68}{68+12} v_g$
 $\sum i_a = 0 = \frac{v_o - v_a}{63k} - \frac{v_a}{30k} = 0 \Rightarrow v_a = .85 v_g; v_o = 10.5V$

(b) Find range of v_g for linear operation ($|v_o| < 12V$)
 Combining eqs. above, $\frac{v_o}{63k} - (\frac{1}{63k} + \frac{1}{30k})(\frac{68}{80} v_g) = 0$
 $\Rightarrow |v_g| \leq 4.55V$ to keep $|v_o| \leq 12V$

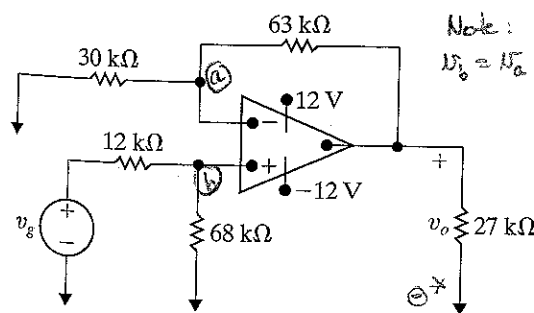


(c) For $v_g = 2V$, $\neq 63k \rightarrow R$, find R for saturation ($|v_o| = 12V$)
 $\frac{\pm 12}{R} - (\frac{1}{R} + \frac{1}{30k})(\frac{68}{80} \cdot 2) = 0$ Choose $v_o = 12V$ for $R > 0$.
 $\Rightarrow R = 182\Omega$

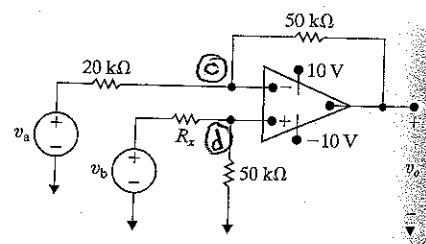4. 5.38 Find R for $CMRR \geq 1000$. Using eqs. 5.29 & 5.30,
 $A_{cm} = \frac{R_a R_d - R_b R_c}{R_a (R_c + R_d)}$ w/ $R_a = 20k\Omega$, $R_b = R_c = 50k\Omega$, $R_c = R_x$
 $A_{dm} = \frac{R_d (R_a + R_b) + R_b (R_c + R_d)}{2 R_a (R_c + R_d)}$
 $\Rightarrow \frac{A_{dm}}{A_{cm}} = \frac{120 + R_x}{2(20 - R_x)} = \pm 1000$
 or $19.93k\Omega \leq R_x \leq 20.07k\Omega$



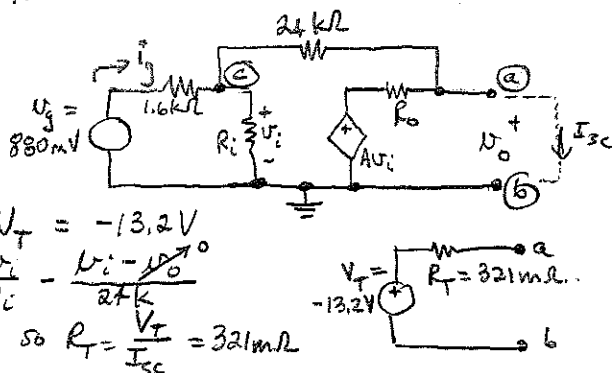5. 5.41 (a) Find Thevenin equiv. @ a, b for $v_s = 880mV$,
 $R_i = 500k\Omega$, $R_o = 2k\Omega$, $A = 10^5$

$V_T = V_{oc} = v_o$: $\sum i = 0 = \frac{.88 - v_i}{1.6k} - \frac{v_i}{R_i} - \frac{v_i - v_o}{24k}$
 $\neq \sum i = 0 = \frac{v_i - v_o}{24k} - \frac{v_o - A v_i}{R_o}$; sub in $A, R_i, R_o \Rightarrow V_T = -13.2V$
 $I_{sc} =$ current when a, b shorted. Now $\sum i = 0 = \frac{.88 - v_i}{1.6k} - \frac{v_i}{R_i} - \frac{v_i - v_o}{24k}$
 $\neq \sum i = 0 = \frac{v_i}{24k} - \frac{A v_i}{R_o} - I_{sc} = 0 \Rightarrow I_{sc} = -41.1A$ so $R_T = \frac{V_T}{I_{sc}} = 321m\Omega$



(b) What is output resistance? Find by applying V_{test} , I_{test} @ output -- equiv to Thevenin calc.

(c) If $R_L = 330\Omega$, find input resistance seen by source.

Now $\sum i = \frac{.88 - v_i}{1.6k} - \frac{v_i}{R_i} - \frac{v_i - v_o}{24k} = 0 \neq \sum i = \frac{v_i - v_o}{24k} - \frac{v_o - A v_i}{R_o} - \frac{v_o}{R_L} = 0$

Plug in again for A, R_i, R_o & solve simultaneously for $v_i = .942mV \Rightarrow i_g = \frac{.88 - .000942}{1.6k} \approx 550\mu A$
 $R_{in} = \frac{v_g}{i_g} \approx 1.602k\Omega$