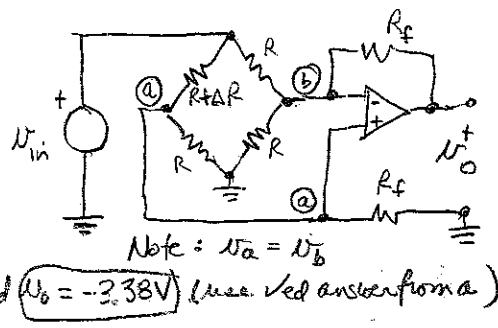


3.6.33 $i_o = 5e^{-2000t} (2 \cos 4000t + \sin 4000t) \text{ A}; t \geq 0^+$. Find $v_1(t), v_2(t)$ @ $t=0^+$.
 $v_R = 40 i_o \Rightarrow v_R(0^+) = 400 \text{ V}; v_L = 0.01 \frac{di_o}{dt} \Rightarrow v_L(0^+) = 0.01(4000) + 0.01(-2000)(2) = 0$
 $v_C = v_1$ @ $t=0^+ \Rightarrow v_1 = v_C = -v_R = 400 \text{ V} \Rightarrow v_1 = 400 \text{ V}, v_2 = 0 \text{ @ } t=0^+$

4.6.33 $i_o = 1.5e^{-16000t} - 0.5e^{-4000t}$ $v_C(0) = -50 \text{ V}$. Find $v_o(t \geq 0)$. ($v_C = -v_o = -v_L$)
 $v_C = \frac{1}{C} \int i_C dt = -\frac{1}{0.025(10^{-6})} \int_0^t (1.5e^{-16000t} - 0.5e^{-4000t}) dt + v_C(0) = 150e^{-16000t} - 200e^{-4000t} - 50 \text{ V}$
 $v_L = L \frac{di_o}{dt} = 0.025(-16000(1.5)e^{-16000t} - 0.5(-4000)e^{-4000t}) = -600e^{-16000t} + 50e^{-4000t} \text{ V}$
 $v_o = v_C - v_L = 750e^{-16000t} - 250e^{-4000t} \text{ V}; t \geq 0$

5.6.50 For all $v_C(0^-) = 0$, Find change in voltage if person touches lamp.
 No finger, $v(t) = \frac{10}{20} v_s(t)$ for 10 pF caps .
 w/ finger & $C_p = \text{cap of person}$, $C = \frac{100(10)}{100+10} \text{ pF} = 9.09 \text{ pF}; C_{||} = C + C_p = 19.09 \text{ pF}$
 so $v(t) = \frac{10}{29.09} v_s = .34 v_s \Rightarrow \Delta v(t) = 0.5 v_s - 0.34 v_s = 0.16 v_s$

1. 5.49 a. Show: for $\Delta R \ll R$, $v_o \approx \frac{R_f (R + R_f)}{R^2 (R + 2R_f)} (-\Delta R) v_{in}$.
 $\sum i_a = \frac{v_{in} - v_a}{R + \Delta R} - \frac{v_a}{R} - \frac{v_a}{R_f} = 0$ Solve simultaneously $\Rightarrow$
 $\sum i_b = \frac{v_{in} - v_a}{R} - \frac{v_a}{R} + \frac{v_o - v_a}{R_f} = 0 \Rightarrow v_o = \frac{-R_f (\Delta R) (R + R_f)}{R [R(R + \Delta R) + R_f(R + \Delta R) + R R_f]} v_{in}$
 or $v_o \approx \frac{-R_f (\Delta R) (R + R_f)}{R^2 (R + 2R_f)} v_{in}$ ✓



c. Find actual v_o . (use /) $\Rightarrow v_o = -3.37$

2. 5.52 Repeat 5.49 if the variable resistor $R + \Delta R$ becomes $R - \Delta R$.
 a. Find v_o if $\Delta R \ll R$. Using prev. results from 5.49, $\rightarrow v_o = \frac{R_f (\Delta R) (R + R_f)}{R [R(R + \Delta R) + R_f(R + \Delta R) + R R_f]} v_{in}$

b. % error in v_o as a function of R, R_f , & ΔR ?
 Approx $\propto R[R(R - \Delta R) + R_f(R - \Delta R) + R R_f]$; Actual $\propto R^2(R + 2R_f)$
 $\text{Error} = \frac{R[R(R - \Delta R) + R_f(R - \Delta R) + R R_f] - R^2(R + 2R_f)}{R^2(R + 2R_f)} = \frac{-\Delta R(R + R_f)}{R(R + 2R_f)} = \text{Error}$
 c. If $R - \Delta R = 9.81 \text{ k}\Omega$, w/ same values of R, R_f , & v_{in} . Find approx v_o . $R - \Delta R = 9.81 \text{ k}$,
 Then $v_o \approx 6.77 \text{ V}$ d. Error for $9.81 \text{ k}\Omega$ is -0.96% $\Delta R = R - 9.81 \text{ k} = 0.19 \text{ k}\Omega$

7. 7.4 $v(t) = 400e^{-5t} \text{ V } t \geq 0^+$; $i(t) = 10e^{-5t} \text{ A}$
 a. Find $R = \frac{v(0)}{i(0)} = 40 \Omega$
 b. Find $\tau = 1/5 \text{ s} = 200 \text{ ms}$
 c. Find $L = R\tau = 40(200 \text{ ms}) = 8 \text{ H}$
 d. Find $w(0) = \frac{1}{2} L i(0)^2 = \frac{1}{2}(8)(100) = 400 \text{ J}$
 e. Find time to dissipate 80% of initial stored energy (20% left)
 $\frac{1}{2} 8 (100e^{-10t})^2 = 0.2(400) \Rightarrow t = 160.9 \text{ ms}$

6. 7.3 Solving @ $t = 0$

a. $i_L(0^-) = 0$
 b. $i_L(0^-) = \frac{120}{120} \left(\frac{12}{10 + (120 \parallel 60)} \right) ; (120 \parallel 60) = 40 \Rightarrow i_L(0^-) = \frac{180(10+40)}{120(12)} = 160 \text{ mA}$
 c. $i_L(0^+) = \frac{120}{120} \left(\frac{12}{10 + (120 \parallel 60)} \right) - i_L(0^-) ; i_L(0^+) = i_L(0^-) \Rightarrow i_L(0^+) = 65 \text{ mA}$
 d. $i_L(0^+) = i_L(0^-) = 160 \text{ mA}$
 e. $i_L(\infty) = \frac{120}{160} \left(\frac{12}{10+30} \right) = 22.5 \text{ mA}$

f. $i_L(\infty) = 0$
 g. $i_L = i_{Lp} + i_{Lh} = 0 + A e^{-Rt/L}$
 h. $i_L(0^-) = 0$
 i. $i_L(0^+) = -i_{Rp}(0^+)$ (since RL now shorted) or $i_L(0^+) = -20(i_L(0^+)) = -3.2 \text{ V}$
 j. $i_L(\infty) = 0$
 k. $i_L(t) = i_{Lp} + i_{Lh} = 0 + A e^{-200t}$
 l. $i_L(t) = -3.2 e^{-200t} \text{ V} ; t \geq 0^+$
 m. $i_L(0) = A = 160 \text{ mA} ; \frac{R}{L} = 200 \Rightarrow L = 160 \text{ e}^{-200t} \text{ mA}$
 n. $i_L(0) = 160 \text{ e}^{-200t} \text{ mA}$
 o. $i_L(0) = 160 \text{ e}^{-200t} \text{ mA} ; t \geq 0^+$