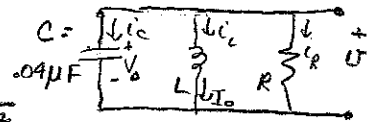


1.8.7 $v(t) = 100 e^{-20000t} [\cos 15000t - 2 \sin 15000t] V; t \geq 0$

b. Find R $Y(s) = \frac{1}{R} + \frac{1}{sL} + sC = \frac{s^2RLC + sL + R}{sLR} = \frac{1}{Z(s)}$

so char eq is $s^2 + s(\frac{1}{RC}) + \frac{1}{LC} = 0 \Rightarrow s = -\frac{1}{2RC} \pm j\sqrt{\frac{1}{LC} - (\frac{1}{2RC})^2} = -\alpha \pm j\omega = -20000 \pm j15000$

$\frac{1}{2RC} = 20000 \Rightarrow R = 625 \Omega$



a. $\frac{1}{LC} - (\frac{1}{2RC})^2 = (15000)^2$; use R from above $\Rightarrow L = 40 \mu H$

c. Find $V_0 = v(0) = 100 V$

d. Find $I_0 = i_L(0) = -i_R(0) - i_C(0) = -\frac{v(0)}{R} - C \frac{dv}{dt} \Big|_{t=0} = \frac{-100}{625} - 0.04(100)[-20000 - 30000] = 40 mA$

e. $i_L(t) = -i_R(t) - i_C(t) = -\frac{v(t)}{R} - C \frac{dv(t)}{dt} = e^{-20000t} [40 \cos 15000t + 220 \sin 15000t] A; t \geq 0$

2. 8.12 Same circuit as in 8.7. $L = 12.5 H, C = 3.2 \mu F, R$ gives critical damping. $V_0 = 100 V, I_0 = 6.4 mA$

a. Find R. (Use $Z(s)$ from above.) For critical damping, $\frac{1}{LC} = (\frac{1}{2RC})^2 \Rightarrow R = 31.25 k\Omega$

b. Find $v(t) = A_1 e^{-t/2RC} + A_2 t e^{-t/2RC} = A_1 e^{-5000t} + A_2 t e^{-5000t}$

$v(0) = 100 = A_1$, $\frac{dv}{dt} \Big|_{t=0} = \frac{i_C(0)}{C} = -\frac{(i_R(0) + i_L(0))}{C} = -\frac{v(0)}{RC} - \frac{I_0}{C} = -3(10^6) V/s$

$\Rightarrow \frac{dv}{dt} \Big|_{t=0} = -3(10^6) = -5000A_1 + A_2 \Rightarrow A_2 = -2.5(10^6)$

$v(t) = 100 e^{-5000t} - 2.5(10^6) t e^{-5000t} V; t \geq 0$

c. Find $v(t)$ when $i_C(t) = 0$. $i_C = C \frac{dv}{dt}$; $\frac{dv}{dt} = -5(10^5) e^{-5000t} - 2.5(10^6) e^{-5000t} - 5(2.5)(10^9) t e^{-5000t}$

$\frac{dv}{dt} = 0$ when $-5(10^5) - 2.5(10^6) - 12.5(10^9)t = 0$ or $@ t = 240 \mu s$


$v(240 \mu s) = -150.6 V$ $w(240) = \frac{1}{2} L i_L^2(240 \mu s) + \frac{1}{2} C v_C^2(240 \mu s)$

d. % of energy remaining @ $t = 240 \mu s$ $w(0) = \frac{1}{2} L i_L^2(0) + \frac{1}{2} C v_C^2(0)$

$v = w$ so plug in $t=0$ & $t=240 \mu s$ to above eq for w

@ $t=240 \mu s, i_C = 0$ so $i_L = -i_R = -\frac{v(240 \mu s)}{R}$, & $i_L(0)$ is given in problem statement: $6.4 mA$

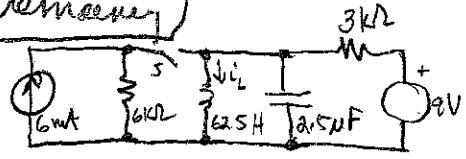Plugging all in $\Rightarrow \frac{145 \mu J + 36.3 \mu J}{256 \mu J + 16 \mu J} \Rightarrow \sim 66.7\% \text{ remaining}$



3. 8.23 S open for a long time; closes @ $t = 0$. Find $i_L(t)$

@ $t = 0^-$, $v_C(0^-) = 0, i_L(0^-) = 3 mA$. @ $t \rightarrow \infty$, $i_L(t \rightarrow \infty) = (6 + 3) mA = 9 mA = I_p$

To find i_L , redraw circuit (remove sources) & find $Z(s) \Rightarrow \frac{6k \parallel \frac{1}{sC}}{3k} = \frac{6k}{1 + s6kC} = \frac{6k}{1 + 3.75s} = \frac{6k}{s + 266.7} = 2k \parallel \frac{1}{sC}$

$Z(s) = sL + \frac{R + 1/sC}{sRC + 1} = \frac{s^2RLC + sL + R}{sRC + 1}$

For homogeneous current, $s^2 + s(\frac{1}{RC}) + \frac{1}{LC} = 0 \Rightarrow s = -100 \pm 60$ (both real)

$i_L(t) = I_p + A_1 e^{-40t} + A_2 e^{-160t}$ (I_p as above)


$i_L(0) = 3m = 9m + A_1 + A_2$; $\frac{di_L}{dt} = \frac{v_L(0^+)}{L} = \frac{v_C(0^+)}{L} = \frac{v_C(0^-)}{L} = 0 = -40A_1 - 160A_2$

$A_1 = -8 mA, A_2 = 2 mA$

$i_L(t) = 9 - 8e^{-40t} + 2e^{-160t} mA; t \geq 0$

Solve simultaneously \Rightarrow

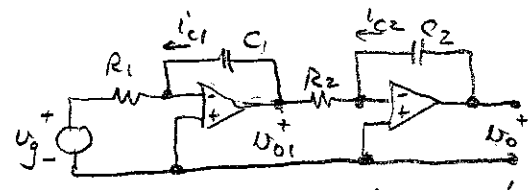4.8.51 $\sum i = C_1 \frac{d}{dt}(U_{o1}-0) + \frac{U_q-0}{R_1} = 0$ ①
 ② $\sum i = C_2 \frac{d}{dt}(U_o-0) + \frac{U_{o1}-0}{R_2} = 0$ ← $\frac{d}{dt}$ of ① ≠ sub into



$\frac{d^2 U_o}{dt^2} = \frac{1}{R_1 C_1 R_2 C_2} U_q = 250 U_q$

$0 \leq t < 0.05s$

$U_q = 80mV \Rightarrow \frac{d^2 U_o}{dt^2} = 20 \Rightarrow U_o(t) = 10t^2 + C_1 t + C_2$ for no initial energy storage $C_1 = 0$ gives $U_o(0) = 0$
 $C_2 = 0$ gives $\frac{dU_o}{dt}|_{t=0} = \frac{U_q}{R_1 C_1} = 0$

eq ① $\Rightarrow \frac{dU_{o1}}{dt} = \frac{-U_q}{R_1 C_1} = -20 U_q = -1.6 \Rightarrow U_{o1}(t) = -1.6t + C_3$

$0.05 \leq t < t_{set}$

$\frac{d^2 U_o}{dt^2} = 250 U_q = -10 \Rightarrow U_o = -5t^2 + C_1' t + C_2'$ $C_2' = U_o(0.05) = -3.75V$ since $U_o = U_{o2}$ can't change
 $\frac{dU_{o1}}{dt} = -20 U_q = 0.8 \Rightarrow U_{o1} = 0.8t + C_3'$ $C_3' = U_{o1}(0.05) = -1.2V$ since $U_{o1} = U_{c1}$ can't change

still need C_1' . Note $\frac{dU_o}{dt}|_{t=0.05} = -10t + C_1' = \frac{i_{c2}(0^+)}{C_2} = \frac{0 - U_{o1}(0.05)}{R_2} = 15$


$0 \leq t < 0.05s : U_o(t) = 10t^2 V, U_{o1}(t) = -1.6t V$
 $0.05s \leq t < t_{set} : U_o(t) = -5t^2 + 15t - 3.75 V ; U_{o1}(t) = 0.8t - 1.2 V$

⑥ $U_o|_{max} = -12.5 V = -5t_{set}^2 + 15t_{set} - 3.75 \Rightarrow$ solve quadratic for $t_{set} = 3.5s$
 check that U_{o1} is not saturated : $U_{o1}(t_{set}) = 1.6 V$ ✓ ok.

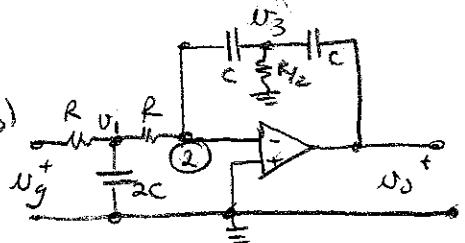5. 8.56

$\sum i = 0 = \frac{U_q - U_1}{R} - 2C \frac{dU_1}{dt} - \frac{U_1}{R} = 0$

$\sum i = 0 = \frac{U_1}{R} + C \frac{dU_3}{dt} \Rightarrow \sum i = 0 = C \frac{d}{dt}(-U_3) - \frac{U_3}{R} - C \frac{d}{dt}(U_3 - U_o)$



① $\frac{dU_1}{dt} + \frac{U_1}{RC} = \frac{U_q}{2RC}$

② $\frac{dU_3}{dt} = -\frac{1}{RC} U_1 \Rightarrow U_1 = -RC \frac{dU_3}{dt}$ Plug ② into ① for U_1 .
 Take $\frac{d}{dt}$ ② to find $\frac{d^2 U_3}{dt^2}$ & plug into ①

③ $\frac{dU_3}{dt} + \frac{U_3}{RC} = -\frac{1}{2} \frac{dU_o}{dt}$ Take $\frac{d}{dt}$ ③

eqs 1 & 2 become $-RC \frac{d^2 U_3}{dt^2} - \frac{dU_3}{dt} = \frac{U_q}{2RC} \Rightarrow \frac{d^2 U_3}{dt^2} + \frac{1}{RC} \frac{dU_3}{dt} = -\frac{U_q}{2R^2 C^2}$
 eq 3 becomes $\frac{d^2 U_3}{dt^2} + \frac{1}{RC} \frac{dU_3}{dt} = \frac{1}{2} \frac{d^2 U_o}{dt^2}$ (LHS are the same)

so $\frac{d^2 U_o}{dt^2} = -\frac{U_q}{R^2 C^2}$

b. The same when $R_1 C_1 = R_2 C_2 = RC$

c. Integrate 2x using just 1 op amp

6. a. long time : $15V$ $i_L = \frac{15}{3} = 5A$ $U_C = 15V, i_C = \frac{15}{3} = 5A$

b. $t=0^+ i_L = 5A, U_C = 15V, i = 0$ since all of U drops across C & none across left R $i_C = -i_L = -5A$

c, d. $Z(s) = 2 + [(s+3) \parallel \frac{1}{s(0.5)}] = 2 + \frac{(s+3)/0.5}{s+3+\frac{1}{0.5s}} = 2 + \frac{s^2+4s+5}{s^2+3s+2}$ For i use $U_{o1} \Rightarrow S = -2 \pm j$

$i_{Lp} = \frac{15}{3+2} = 3A$

$i_L = i_{Lh} + i_{Lp} = Ae^{-2t} \cos(t+\beta) + 3$

$i_L(0) = 0 = A \cos \phi + 3$
 $\frac{di_L}{dt}|_{t=0} = \frac{d}{dt}(\frac{15-U_C}{2}) = -\frac{1}{2} \frac{dU_C}{dt} = -\frac{1}{2} \frac{15}{RC} = 5A/s$
 $= -2A \cos \phi - A \sin \phi$

$i_L(t) = 3 - 3.16 e^{-2t} \cos(t - 184^\circ) A \quad t \geq 0$